

- **Problem:** an n -bit register based on latches (resp. flip-flops) is limited in that
1. each latch (resp. flip-flop) in the register needs a relatively large number of transistors, which limits the viable capacity (i.e., n), and
 2. the register is not addressable, i.e.,
 - an **address** (or **index**) allows dynamic rather than static reference to some stored datum, so
 - by analogy, in a C program

Listing

```

1  int A0, A1, A2, A3;
2
3  A0 = 0;
4  A1 = 0;
5  A2 = 0;
6  A3 = 0;
```


Listing

```

1  int A[ 4 ];
2
3  A[ 0 ] = 0;
4  A[ 1 ] = 0;
5  A[ 2 ] = 0;
6  A[ 3 ] = 0;
```

we *have* the left-hand side, but we *want* the right-hand side.

 - **Solution:** a **memory** component, i.e.,



such that

- MEM has a capacity of $n = 2^{n'}$ addressable words, and
- each such word is w bits.

► Agenda:

1. memory *cells*,
2. memory *devices*,

noting there are various ways to classify memories, e.g.,

1. volatility:
 - **volatile**, meaning the content is lost when the component is powered-off, or
 - **non-volatile**, meaning the content is retained even after the component is powered-off.
2. interface type:
 - **synchronous**, where a clock or pre-determined timing information synchronises steps, or
 - **asynchronous**, where a protocol synchronises steps.
3. access type:
 - random versus constrained (e.g., sequential) access to content,
 - **Random Access Memory (RAM)** which we can read from *and* write to, and
 - **Read Only Memory (ROM)** which, as suggested by the name, supports reads only.
4. ...


but we'll focus exclusively on a volatile, synchronous RAM.

An Aside: some history



- ▶ The EDSAC used **delay line** memory, where the rough idea is:
 - ▶ Each “line” is a tube of mercury (or something else in which sound waves propagate fairly slowly).
 - ▶ Put a speaker at one end to store sound waves into the line, and a microphone at the other to read them out.
 - ▶ Values are stored in the sense the corresponding waves take time to propagate; when they get to one end they are either replaced or fed back into the other.
- ▶ This is **sequential access** (cf. **random access**): you need to *wait* for the data you want to appear!

An Aside: some history

 

- ▶ The Whirlwind used **magnetic-core** memory, where the rough idea is:
 - ▶ The memory is a matrix of small magnetic rings, or “cores”, which can be magnetically polarised to store values.
 - ▶ Wires are threaded through the cores to control them, i.e., to store or read values.
 - ▶ The magnetic polarisation is retained, so core memory is non-volatile!
- ▶ You might still hear main memory termed **core memory** (cf. **core dump**) which is a throw-back to this technology.

https://en.wikipedia.org/wiki/File:Project_Whirlwind_-_core_memory,_circa_1951_-_detail_1.JPG

Part 1: memory cells (1)

Comparison

Static RAM (SRAM) is

- ▶ manufacturable in lower densities (i.e., smaller capacity),
- ▶ more expensive to manufacture,
- ▶ fast(er) access time (resp. lower access latency),
- ▶ easy(er) to interface with,
- ▶ ideal for latency-optimised contexts, e.g., as cache memory.

Comparison


Dynamic RAM (DRAM) is

- ▶ manufacturable in higher densities (i.e., larger capacity),
- ▶ less expensive to manufacture,
- ▶ slow(er) access time (resp. higher access latency),
- ▶ hard(er) to interface with,
- ▶ ideal for capacity-optimised contexts, e.g., as main memory.

Part 1: memory cells (2)

An SRAM cell

Circuit

 


► Idea:

- internally, the cell is essentially two NOT gates,
- bl and $\neg bl$ are the **bit lines** (via which the state is accessed),
- wl is the **word line** (which controls access to the state),
- a “6T SRAM cell” requires 6 transistors (cf. ~ 20 or so for a D-type latch).

Part 1: memory cells (2)

An SRAM cell

Circuit

 


► Idea:

- internally, the cell is essentially two NOT gates,
- bl and $\neg bl$ are the **bit lines** (via which the state is accessed),
- wl is the **word line** (which controls access to the state),
- a “6T SRAM cell” requires 6 transistors (cf. ~ 20 or so for a D-type latch).

Part 1: memory cells (3)

A DRAM cell

Circuit

 

- ▶ **Idea:**
 - ▶ internally, the cell is essentially one transistor and one capacitor,
 - ▶ *bl* is the **bit line** (via which the state is accessed),
 - ▶ *wl* is the **word line** (which controls access to the state),
 - ▶ the capacitor
 1. discharges and charges (relatively) slowly,
 2. discharges when the cell is read, *and* also over time even if it's not read; this implies a need to **refresh** it.

Part 2: memory cells $\leadsto$ memory devices (1)

► **Concept:** a **memory device** is constructed from (roughly) three components

1. a **memory array** (or matrix) of replicated cells with

- r rows, and
- c columns

meaning a $(r \cdot c)$ -cell capacity,

2. a **row decoder** which given an address (de)activates associated cells in that row, and

3. a **column decoder** which given an address (de)selects associated cells in that column

plus additional logic to allow use (depending on cell type), e.g.,

1. **bit line conditioning** to, e.g., ensure the bit lines are strong enough to be effective, and
2. **sense amplifiers** to, e.g., ensure output from the array is usable.

Part 2: memory cells $\leadsto$ memory devices (2)

An SRAM device: design

► (Typical, or exemplar) **design**: an **SRAM device**.

1. interface:

- auxiliary pin(s) for power and so on,
- D , a single 1-bit **data pin**,
- A , a collection of n' **address pins** where A_i is the i -th such pin,
- a **Chip Select (CS)** pin, which enables the device,
- a **Output Enable (OE)** pin, which signals the device is being read from,
- a **Write Enable (WE)** pin, which signals the device is being written to.

Part 2: memory cells $\leadsto$ memory devices (2)

An SRAM device: design

- (Typical, or exemplar) **design**: an **SRAM device**.

2. usage:

Algorithm (SRAM-READ)

Having performed the following steps

- drive the address onto A ,
- set $WE = \text{false}$, $OE = \text{true}$ and $CS = \text{true}$,

1-bit of data is read and made available on D , then we set $CS = \text{false}$.

Algorithm (SRAM-WRITE)

Having performed the following steps


- drive the data onto D ,
- drive the address onto A ,
- set $WE = \text{true}$, $OE = \text{false}$ and $CS = \text{true}$,

1-bit of data is written, then we set $CS = \text{false}$.

Part 2: memory cells $\leadsto$ memory devices (3)

An SRAM device: implementation

Example (an n -cell SRAM device, for $n = 2^{n'}$)

 

Part 2: memory cells $\leadsto$ memory devices (4)

An SRAM device: implementation



ASI
Austin Semiconductor, Inc.

SRAM
MT5C1001
Limited Availability

1M x 1 SRAM
SRAM MEMORY ARRAY

AVAILABLE AS MILITARY SPECIFICATIONS

- MIL-STD-883C
- MIL-STD-883

FEATURES

- High Speed: 20, 25, 35, and 45
- Battery Backup: 2V data retention
- Low power standby
- Single +5V ($\pm 10\%$) Power Supply
- Easy memory expansion with CE and OE options.
- All inputs and outputs are TTL compatible
- Three-state output

OPTIONS


- **Tuning**
 - 20ns access -20
 - 25ns access -25
 - 35ns access -35
 - 45ns access -45
 - 55ns access -55
 - 70ns access -70*
- **Packaging**
 - Ceramic DIP (400 mil) C No. 109
 - Ceramic LCC EC No. 207
 - Ceramic Flipchip F No. 303
 - Ceramic SOJ DCJ No. 501
- **Operating Temperature Ranges**
 - Industrial (-40°C to +85°C) IT
 - Military (-55°C to +125°C) XT
- 2V data retention low power L

MARKING

For more products and information please visit our web site at www.austinsemiconductor.com

MT5C1001 Rev. 04-10-00

PIN ASSIGNMENT (Top View)

 

GENERAL DESCRIPTION

The MT5C1001 employs low-power, high-performance silicon-gate CMOS technology. Static design eliminates the need for internal clocks or timing modes while CMOS circuitry reduces power consumption and provides for greater reliability.

For flexibility in high-speed memory applications, ASI offers chip enable (CE) and output enable (OE) capability. These enhancements can place the outputs in High-Z for additional flexibility in system design. Writing to these devices is accomplished when write enable (WE) and CE inputs are both LOW. Reading is accomplished when WE remains HIGH while CE and OE go LOW. The devices offer a reduced power standby mode when disabled. This allows system design to achieve low standby power requirements.

The "L" version provides an approximate 50 percent reduction in CMOS standby current (I_{stand}) over the standard version.


All devices operation from a single +5V power supply and all inputs and outputs are fully TTL compatible.



ASI
Austin Semiconductor, Inc.

SRAM
MT5C1001
Limited Availability

FUNCTIONAL BLOCK DIAGRAM

 

TRUTH TABLE

MODE	CE	OE	WE	OUTPUT	POWER
STANDBY	H	H	L	HIGH-Z	STANDBY
READ	L	H	H	ACTIVE	ACTIVE
WRITE	L	L	HIGH-Z	ACTIVE	ACTIVE

PIN ASSIGNMENTS

PIN	ASSIGNMENT
A_0 - A_{15}	Address Inputs
WE	Write Enable
CE	Chip Enable
D	Data Input
Q	Data Output
NC	No Connection
V_{CC}	+5V Power Supply
V_{SS}	Ground

MT5C1001 Rev. 04-10-00

Part 2: memory cells $\leadsto$ memory devices (5)

A DRAM device: interface

► (Typical, or exemplar) **design**: a **DRAM device**.

1. interface:

- auxiliary pin(s) for power and so on,
- D , a single 1-bit **data pin**,
- A , a collection of $n'/2$ **address pins** where A_i is the i -th such pin,
- a **Chip Select (CS)** pin, which enables the device,
- a **Output Enable (OE)** pin, which signals the device is being read from,
- a **Write Enable (WE)** pin, which signals the device is being written to,
- a **Row Address Strobe (RAS)**, which controls the row buffer, and
- a **Column Address Strobe (CAS)**, which controls the column buffer.

Part 2: memory cells $\leadsto$ memory devices (5)

A DRAM device: interface

- (Typical, or exemplar) **design**: a **DRAM device**.

2. usage:

Algorithm (DRAM-READ)

Having performed the following steps

- drive the row address onto A ,
- set $RAS = \text{true}$ to latch row address,
- drive the column address onto A ,
- set $CAS = \text{true}$ to latch column address,
- set $WE = \text{false}$, $OE = \text{true}$ and $CS = \text{true}$,

1-bit of data is read and made available on D , then we set $CS = RAS = CAS = \text{false}$.

Algorithm (DRAM-WRITE)

Having performed the following steps


- drive the data onto D ,
- drive the row address onto A ,
- set $RAS = \text{true}$ to latch row address,
- drive the column address onto A ,
- set $CAS = \text{true}$ to latch column address,
- set $WE = \text{false}$, $OE = \text{true}$ and $CS = \text{true}$,

1-bit of data is written, then we set $CS = RAS = CAS = \text{false}$.

Part 2: memory cells $\leadsto$ memory devices (6)

A DRAM device: implementation

Example (a n -cell DRAM memory device, for $n = 2^{n'}$)

 

Part 2: memory cells $\leadsto$ memory devices (7)

A DRAM device: implementation


AUSTIN SEMICONDUCTOR, INC.

MT4C1004J 883C
4 MEG x 1 DRAM

DRAM

4 MEG x 1 DRAM

FAST PAGE MODE

AVAILABLE AS MILITARY SPECIFICATIONS

- SMD (D62-90622)
- MIL-STD-883C

FEATURES

- Industry standard x1 pinout, timing, functions and packages
- High-performance, CMOS silicon-gate process
- Single +5V 150mA power supply
- Low-power, 25mW standby; 300mW active, typical
- All inputs, outputs and clocks are fully TTL and CMOS compatible
- 1.024-cycle refresh distributed across 16ms
- Refresh modes: **RCS-ONLY**, **CAS-BEFORE-RCS** (CBR), and **HIDDEN**
- FAST PAGE MODE** access cycle
- CBR with **WE** a **HIGH** (REDC) test mode capable via WCA00

OPTIONS

- Timing
- 70ns access
- 80ns access
- 100ns access
- 120ns access

MARKING

	CN	No. 331
Ceramic DIP (600 mil)	C	No. 302
Ceramic LCC	ELCN	No. 202
Ceramic SOJ	ELCJ	No. 204
Ceramic ZIP	CZ	No. 400
Ceramic Gull Wing	ELCG	No. 409

PIN ASSIGNMENT (Top View)

18-Pin DIP



20-Pin ZIP



20-Pin SOJ

20-Pin LCC

20-Pin Gull Wing



*Hidden pins used for NOSE (CNC) & REDUCED

GENERAL DESCRIPTION

The MT4C1004J is a randomly accessed solid-state memory containing 4,096 16-bit words organized in a 16K configuration. During READ or WRITE cycles, each bit is uniquely addressed through the 22 address lines which are connected 11 bits (A0-A10) as a time. **RCS** is used to latch the first 11 bits and **CAS** the latter 11 bits. A READ or WRITE cycle is selected with the **WE** input. A high **HIDDEN** as **WE** dictates READ mode while a logic LOW as **WE** dictates WRITE mode. During a WRITE cycle, data-in (DI) is latched by the

2-23

As an semiconductor, the information on the right is subject to change without notice.


AUSTIN SEMICONDUCTOR, INC.


MT4C1004J 883C
4 MEG x 1 DRAM

boundary. The FAST PAGE MODE cycle is always initiated with a new address strobed in by **RCS** followed by a column address strobed in by **CAS**. **CAS** may be supplied in by holding **RAS** LOW and stroking in different column addresses, thus executing faster memory cycles. Retaining **RAS** HIGH terminates the FAST PAGE MODE operation, returning **RCS** and **CAS** HIGH to terminate a memory cycle and decreases chip stress to a reduced standby level. Also,

the chip is preconditioned for the next cycle during the **RAS** HIGH time. Memory cell data is retained during the next read by maintaining power or reactivating any **RCS** cycle (READ, WRITE, **RCS-ONLY**, **CAS-BEFORE-RCS**, or **HIDDEN** REFRESH) so that all 1.024 combinations of **RCS** addresses (A0-A10) are executed at least every 16ms, regardless of sequence. The **CAS-BEFORE-RCS** cycle will involve the refresh counter for automatic **RCS** addressing.

FUNCTIONAL BLOCK DIAGRAM

FAST PAGE MODE

 

*NOTE: **WE** LOW prior to **CAS** LOW. **EW** detection circuit output is a HIGH (EARLY WRITE) **CAS** LOW prior to **WE** LOW. **EW** detection circuit output is a LOW (LATE WRITE)

2-24

As an semiconductor, the information on the right is subject to change without notice.

Part 2: memory cells $\leadsto$ memory devices (9)

► Concept:

- *externally*, the configuration of a device is described as something like


$$\delta \times \omega \times \beta$$

(plus maybe some timing information) where

- δ relates to capacity, usually measured in (large multiples of) bits,
 - ω describes the width of words, measured in bits, and
 - β is the number of internal **logical banks**.
- *internally*, this implies some organisational choices: for example,
 1. for $\omega > 1$, we replicate the memory device internally to give ω arrays (each copy relates to one bit of a ω -bit word),
 2. for the arrays, r and c can be selected to match physical requirements (e.g., to get “square” or “thin” arrays), and
 3. for $\beta > 1$, each array is split into logical **banks**.


Part 2: memory cells $\leadsto$ memory devices (10)

Example (from a 1-bit to w -bit SRAM device via replication)

 

Part 2: memory cells $\leadsto$ memory devices (11)

 Example (from a 1-bit to w -bit DRAM device via replication)



► Take away points:

1. The initial goal was an n -element memory of w -bit words; the final solution is motivated by divide-and-conquer, i.e.,
 - 1.1 one or more channels, each backed by
 - 1.2 one or more physical banks, each composed from
 - 1.3 one or more devices, each composed from
 - 1.4 one or more logical banks, of
 - 1.5 one or more arrays, of
 - 1.6 many cells
2. The major complication is a large range of increasingly detailed options:
 - lots of parameters mean lots of potential trade-offs (e.g., between size, speed and power consumption),
 - need to take care of detail: there are so many cells, any minor change can have major consequences!
3. Even so, there is just one key concept: we have some cells, and however they are organised we just need to identify and use the right cells given some address.

Additional Reading

- ▶ *Wikipedia: Computer Memory*. URL: https://en.wikipedia.org/wiki/Category:Computer_memory.
- ▶ D. Page. “Chapter 8: Memory and storage”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.3.5: Memory chips”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.
- ▶ A.S. Tanenbaum and T. Austin. “Section 3.3.6: RAMs and ROMs”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012.
- ▶ W. Stallings. “Chapter 5: Internal memory”. In: *Computer Organisation and Architecture*. 9th ed. Prentice Hall, 2013.

References

- [1] [Wikipedia: Computer Memory](https://en.wikipedia.org/wiki/Category:Computer_memory). URL: https://en.wikipedia.org/wiki/Category:Computer_memory (see p. 23).
- [2] D. Page. “Chapter 8: Memory and storage”. In: *A Practical Introduction to Computer Architecture*. 1st ed. Springer, 2009 (see p. 23).
- [3] W. Stallings. “Chapter 5: Internal memory”. In: *Computer Organisation and Architecture*. 9th ed. Prentice Hall, 2013 (see p. 23).
- [4] A.S. Tanenbaum and T. Austin. “Section 3.3.5: Memory chips”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 23).
- [5] A.S. Tanenbaum and T. Austin. “Section 3.3.6: RAMs and ROMs”. In: *Structured Computer Organisation*. 6th ed. Prentice Hall, 2012 (see p. 23).